



Assignment 1

Objective:

- Use I2C communication to store a value in EEPROM and retrieve it every time the microcontroller is reset.

Components:

- ATmega32 microcontroller
- I2C EEPROM
- Resistors
- wires

Circuit Setup:

- Connect EEPROM's SDA and SCL pins to the corresponding I2C pins on the ATmega32.
- Connect pull-up resistors (e.g., 4.7k Ω) to the SDA and SCL lines.
- Connect EEPROM's VCC and GND to the power supply.